



# Basic Circuit Analysis

W. Bolton, "Mechatronics --- Electronic control systems in mechanical and electrical engineering," 5<sup>th</sup> edition, Pearson Education Limited 2012  
J. Edward Carryer, R. Matthew Ohline, Thomas W. Kenny, "Introduction to Mechatronic Design," Prentice Hall 2011, Chap 9  
線上學習網站 : <https://www.electronics-tutorials.ws>  
PowerPoint 中部分圖片擷取和修改自教科書和網路圖片

林沛群  
國立台灣大學  
機械工程學系

## Terminology -1

- **Charge ( $Q$ ):** quantity of charged particles
  - ◆ Unit: Coulomb ( $C$ ),  $1C = 6.24 \times 10^{18}$  charged particles
- **Current ( $I$ ):** number of charged particles that move past any point in an increment of time ---  $\frac{dQ}{dt}$ 
  - ◆ Unit: Ampere ( $A = \frac{C}{s}$ )
- **Voltage ( $V$ ):** strength of the electric field ---  $\frac{dW}{dQ}$ , work done per unit charge
  - ◆ Unit: volt ( $V = \frac{J}{C}$ , work done in moving a coulomb of charge)

## Terminology -2

- Power ( $P$ ): rate at which work is being done

$$P = \frac{\text{work}}{\text{time}} = \frac{\text{joules (J)}}{\text{second(s)}} = \frac{\text{joules}}{\text{coulomb}} \times \frac{\text{coulomb}}{\text{second}} = \frac{J}{C} \times \frac{C}{s} = VI$$

- ◆ Unit: watt ( $W = \frac{J}{s}$ )

- ◆  $1W = 1\frac{J}{s} = 1\frac{Nm}{s} = 1\frac{(kg\frac{m}{s^2})m}{s} = 1\frac{kgm^2}{s^3} \quad (ML^2T^{-3})$

represented in seven SI base units


## Seven SI Base Units

Name	Symbol	Measure	Dimension Symbol
Meter	m	Length	L
Kilogram	kg	Mass	M
Second	s	Time	T
Ampere	A	Electric current	I
Kelvin	K	Thermodynamic temperature	$\Theta$
Mole	mol	Amount of substance	N
Candela	cd	Luminous intensity	J

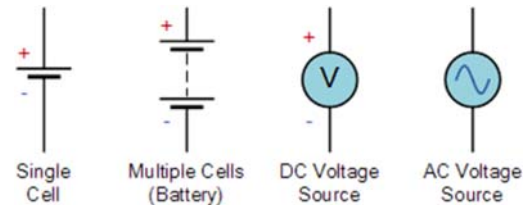
## Terminology -3

- **Voltage source:** an ideal source would deliver a constant voltage independent of current drawn from the source

- ◆ Direct current (DC)
- ◆ Alternating current (AC)



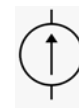- **Current source:** an ideal current source would generate whatever voltage was necessary to produce a constant flow of current



## Terminology -4

- **Circuits**

- ◆ A complete circuit

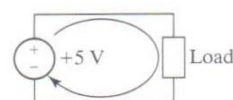


FIGURE 9.2  
The simplest complete circuit.

- ◆ An open circuit

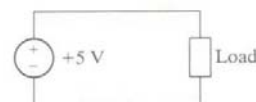


FIGURE 9.3  
In an open circuit, no current flows.


- ◆ A short circuit




FIGURE 9.4  
A short circuit across the voltage source and the load.
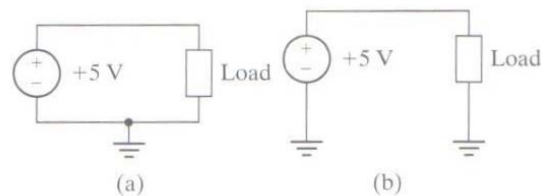
## Terminology -5

- **Shorting:** the process of creating a short circuit  
a transient effect, causing high current to flow
- **Ground:** a common reference point through a circuit and represents the point that will be assigned a value of 0V




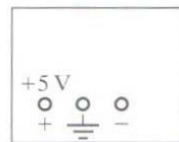- **Floating:** no direct connection to the building ground



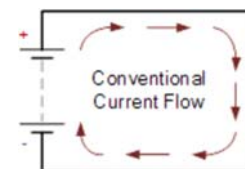
## Electrical Current

- **Conventional current flow**
  - ◆ The flow of positive charge around a circuit, being positive to negative



- **Electron flow**

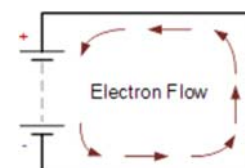- ◆ The actual current flowing in an electrical circuit is composed of electrons that flow from the negative to positive



# Kirchhoff's Law

## □ Kirchhoff's Current (First) Law



- ◆ The sum of all the current entering a node of a circuit is the same as the sum of all the current leaving that same node
- ◆ Conservation principle

$$\Rightarrow \sum_{k=1}^n i_k = 0$$

## □ Kirchhoff's Voltage (Second) Law

- ◆ The sum of the voltage differences around any closed loop in a circuit is zero

$$\Rightarrow \sum_{k=1}^n V_k = 0$$

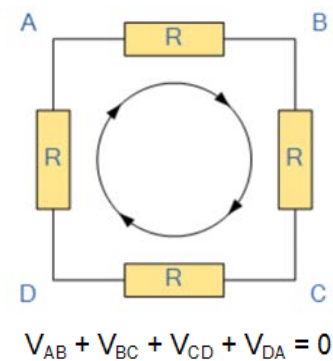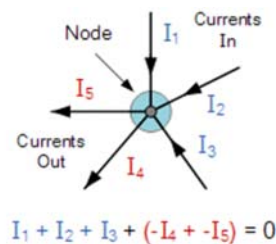

# An Example -1


## □ Ex: A circuit

- ◆ Method 1: Kirchhoff's Laws

$$10 - 10i_1 - 40i_3 = 0$$

$$20 - 20i_2 - 40i_3 = 0$$

$$i_3 = i_1 + i_2$$

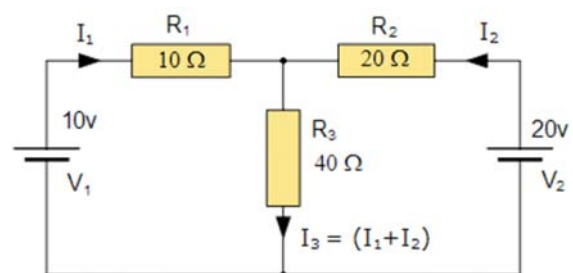

$$\Rightarrow i_1 = \underline{-0.143} \quad i_2 = 0.429 \quad i_3 = 0.286$$


20V battery is charging the 10V battery

## An Example -2

### □ Ex: A circuit
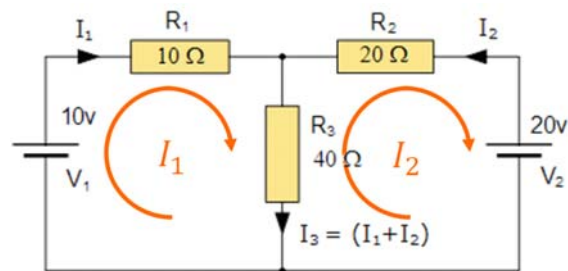
#### ◆ Method 2: Mesh current analysis (or loop analysis or Maxwell's circulating currents)

- Label inside loops in a clockwise direction with circulating currents as the aim to cover all the elements of the circuit at least once



$$I_1 = i_1, I_2 = -i_2$$

$$10 = (10 + 40)I_1 - 40I_2$$

$$-20 = -40I_1 + (20 + 40)I_2$$

$$V = RI$$

$$\Rightarrow I = R^{-1}V = \begin{bmatrix} -0.143 \\ -0.429 \end{bmatrix}$$

## An Example -3

### □ Ex: A circuit


#### ◆ Method 3: Nodal voltage analysis

$$i_1 + i_2 = i_3$$

$$\frac{v_a - v_b}{10} + \frac{v_c - v_b}{20} = \frac{v_b}{40}$$

$$v_a = 10, v_c = 20$$

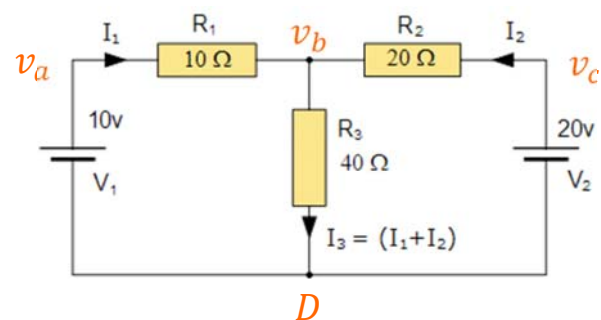
$$\Rightarrow v_b = \frac{80}{7}V \quad i_3 = \frac{2}{7} = 0.286A$$



# Thevenin's Theorem
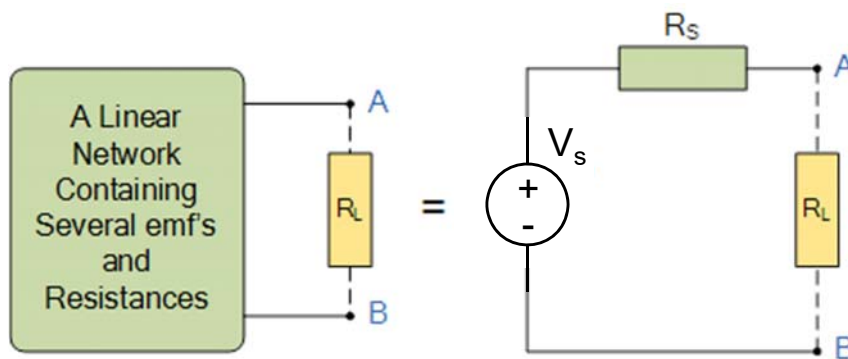
## □ Thevenin's Theorem



- ◆ Any linear circuit containing **several voltages and resistors** can be replaced by just **one** single voltage in series with a single resistance connected across the load



## Revisit the Example -1
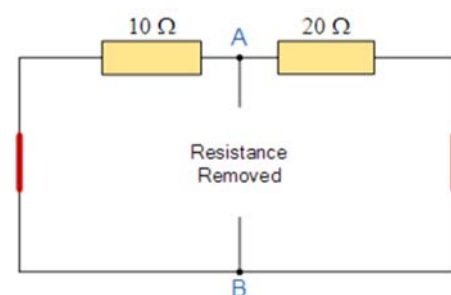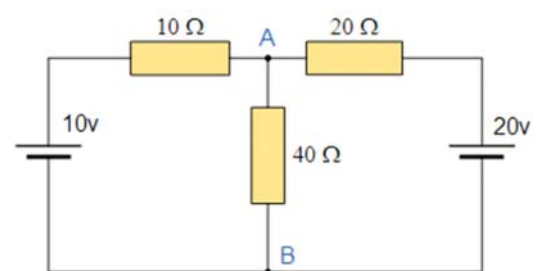
### □ Ex: The circuit

- ◆ Step 1: Remove the load resistor
- ◆ Step 2: Find the equivalent resistor by shorting all voltage sources and opening circuiting all current sources




$$R_{equiv} = \frac{1}{\frac{1}{10} + \frac{1}{20}} = 6.67\Omega$$

## Revisit the Example -2

- ◆ Step 3: Find the equivalent voltage source by the usual circuit analysis


$$I = \frac{V}{R} = \frac{20 - 10}{20 + 10} = 0.33A$$
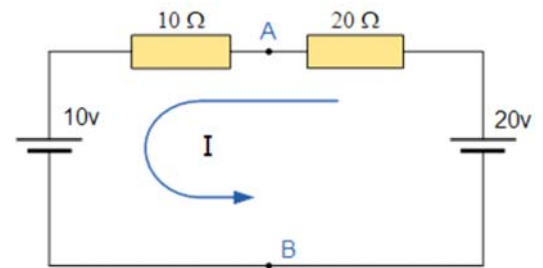
$$V_{AB} = 20 - (20 * 0.33) = 13.33V$$
$$= 10 + (10 * 0.33) = 13.33V$$



- ◆ Step 4: Find the current flowing through the load resistor

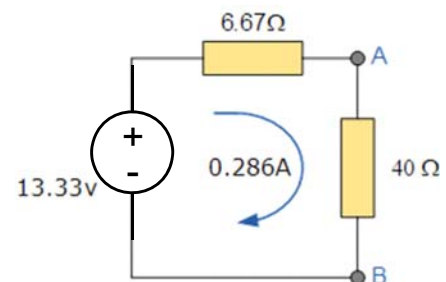
$$I = \frac{V}{R} = \frac{13.33}{6.67 + 40} = 0.286A$$



## Norton's Theorem
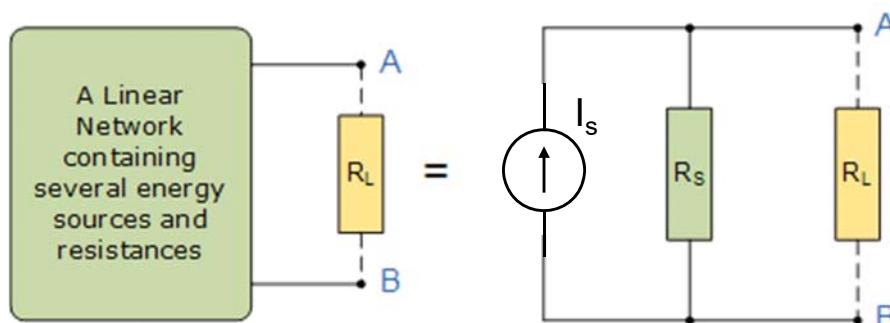
### □ Norton's Theorem

- ◆ Any linear circuit containing several energy sources and resistances can be replaced by a single constant current generator in parallel with a single resistor







## Revisit the Example -3
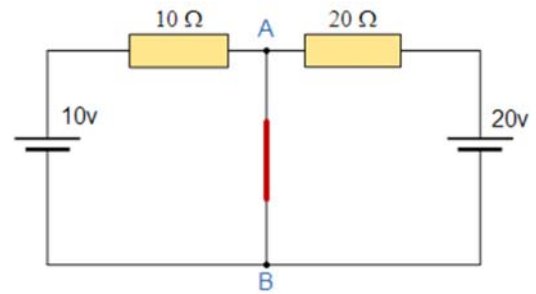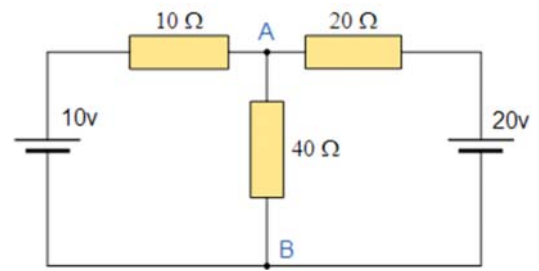
### □ Ex: The circuit

- ◆ Step 1: Remove the load resistor
- ◆ Step 2: Find the equivalent current source by placing a short link on the original load terminals



$$I_{equiv} = \frac{10}{10} + \frac{20}{20} = 2A$$

## Revisit the Example -4



### □ Ex: Revisit the same circuit

- ◆ Step 3: Find the equivalent resistor by shorting all voltage sources and opening circuiting all current sources

$$R_{equiv} = \frac{1}{\frac{1}{10} + \frac{1}{20}} = 6.67\Omega$$

- ◆ Step 4: Find the current flowing through the load resistor

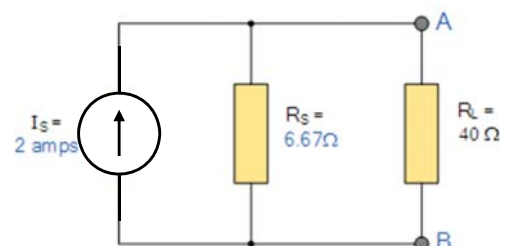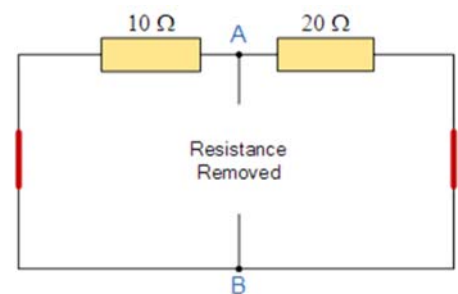
$$I = \frac{6.67}{6.67 + 40} * 2 = 0.286A$$



# Electrical Sources

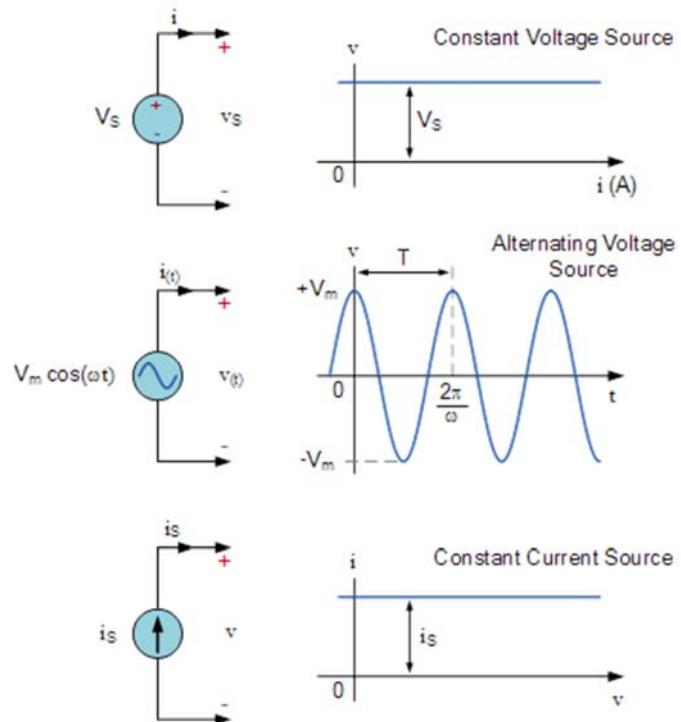
## □ Electrical Sources

- ◆ DC voltage source
- ◆ AC voltage source
- ◆ Current source



# Voltage Sources



## □ Ideal and practical voltage source

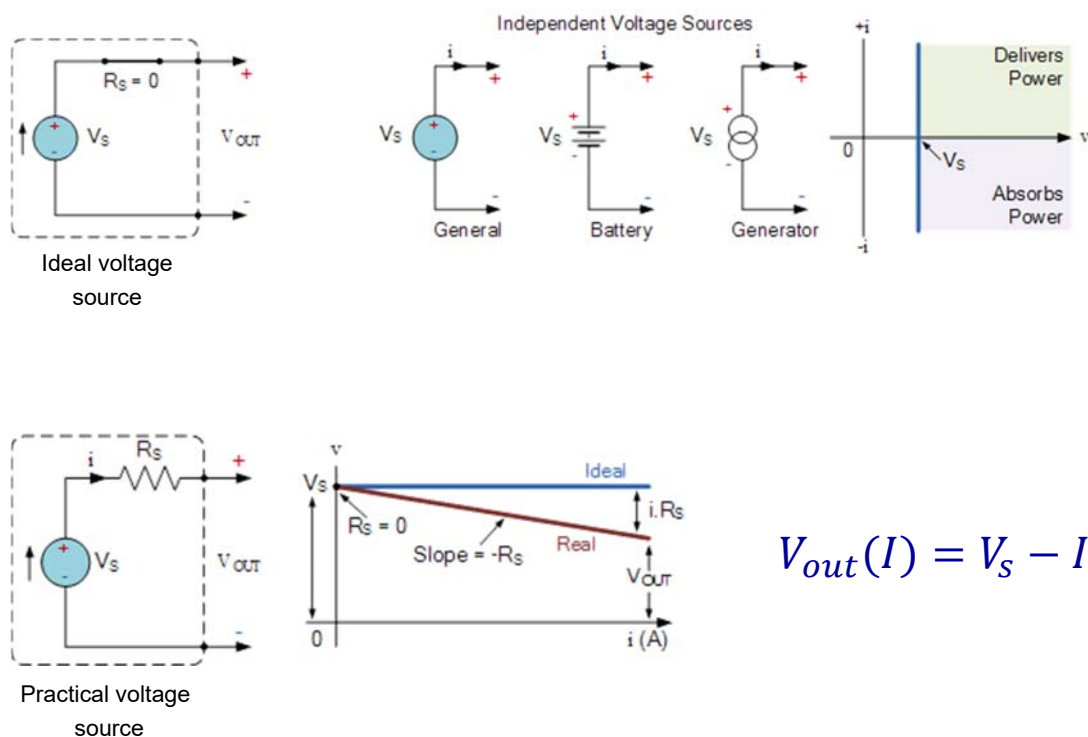

$$V_{out}(I) = V_s - IR_s$$

# Current Sources

## □ Ideal and practical current source

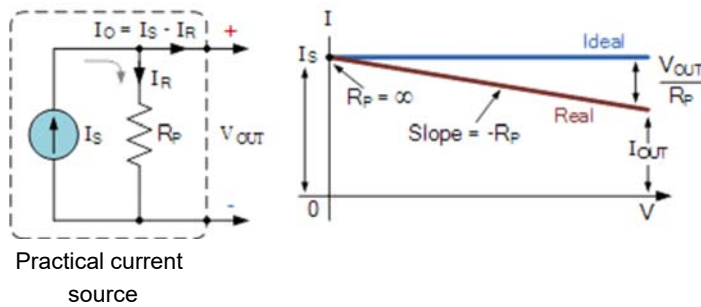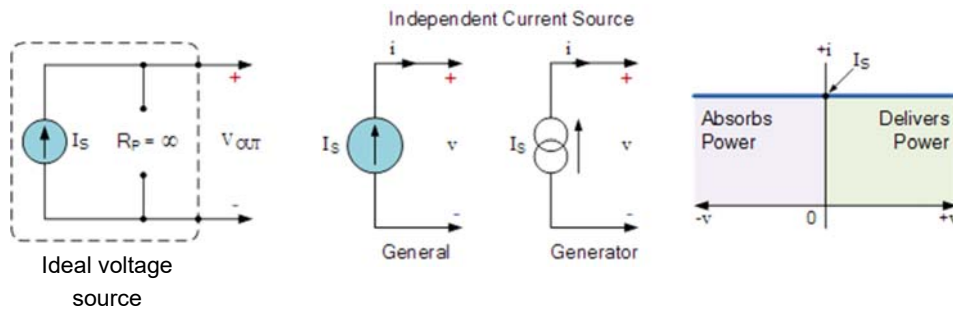

$$I_{out}(V_{out}) = I_s - \frac{V_{out}}{R_p}$$

# The End

## □ Questions?

