

Switches


W. Bolton, "Mechatronics --- Electronic control systems in mechanical and electrical engineering," 5th edition, Pearson Education Limited 2012, Chap 9
J. Edward Carryer, R. Matthew Ohline, Thomas W. Kenny, "Introduction to Mechatronic Design," Prentice Hall 2011
線上學習網站 : <https://www.electronics-tutorials.ws>
PowerPoint 中部分圖片擷取和修改自教科書和網路圖片

林沛群
國立台灣大學
機械工程學系

Switch -1


□ Definition

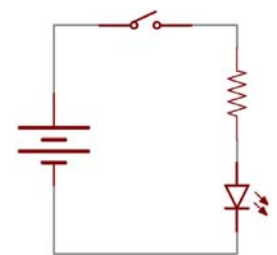- ◆ A component which controls the open-ness or closed-ness of an electric circuit



Reed switch: open or close when exposed to the presence of a magnetic field

Dip switch

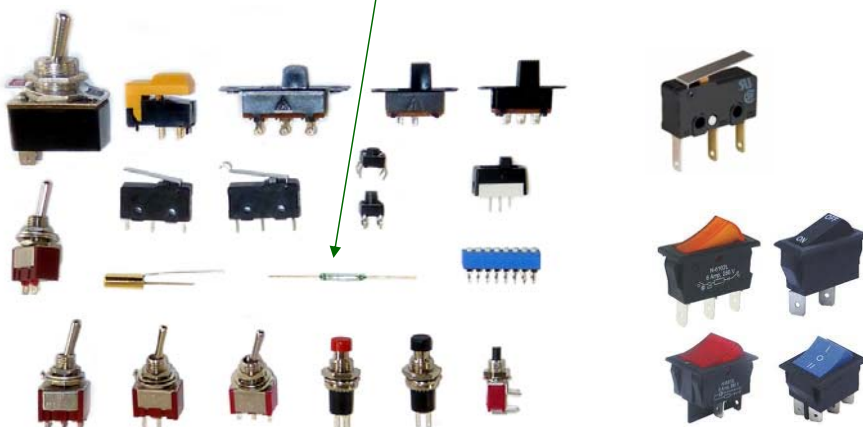


Switch -2

Terminologies

Pole (軸) & throw (切)

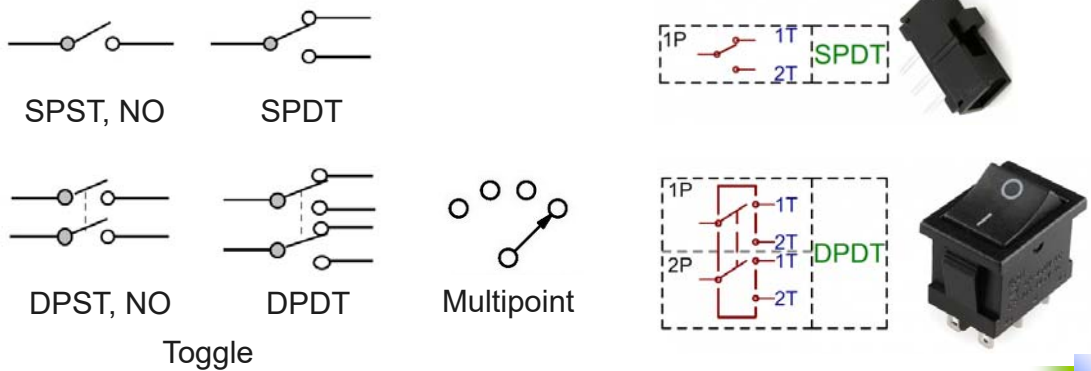
- SPST – Single pole, double throw (單軸單切)
- SPDT – Single pole, double throw (單軸雙切)
- DPST – Single pole, double throw (雙軸單切)
- DPDT – Single pole, double throw (雙軸雙切)



Switch -3

Terminologies

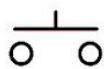
Normally open (NO, 常開) vs. normally closed (NC, 常閉)



Momentary vs. maintained



Change over

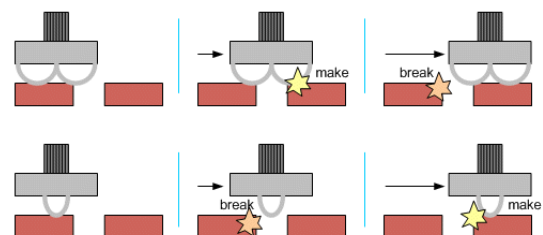- Make-before-break (MBB) – rarely used
- Break-before-make (BBM)



Switch -4


Ex: Illuminated switches

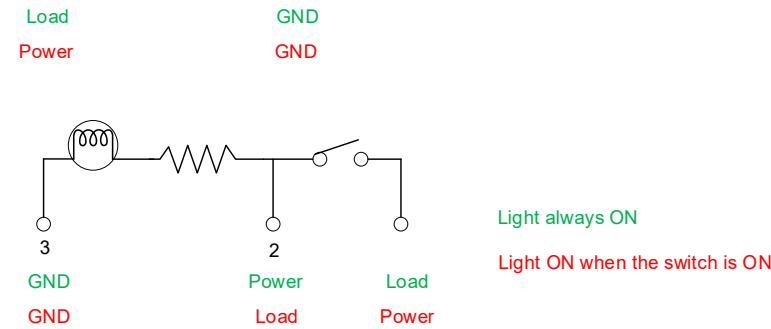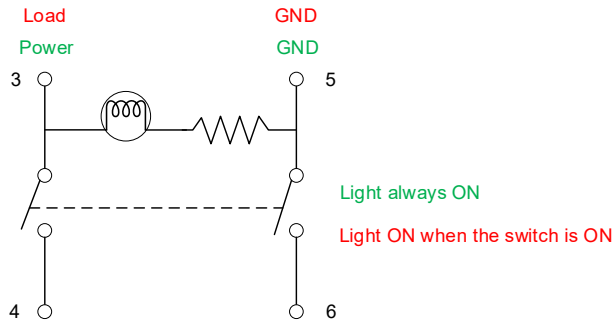

Switch -5

Ex: Staircase wiring circuit


$$T = A\bar{B} + \bar{A}B$$

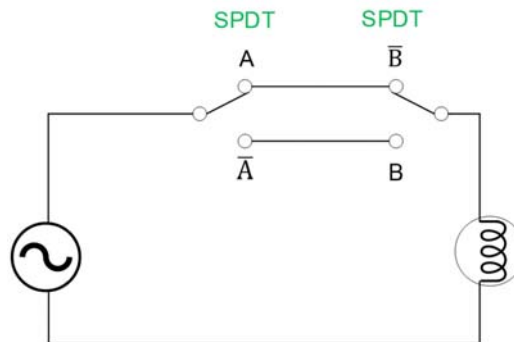

2-way switch, SPST



3-way switch, SPDT

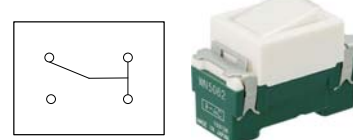


Electro-Mechanical Relay -1

□ Definition

- ◆ A electrically operated switch in which changing a current in one electric circuit switches a current on or off in another circuit

□ Applications

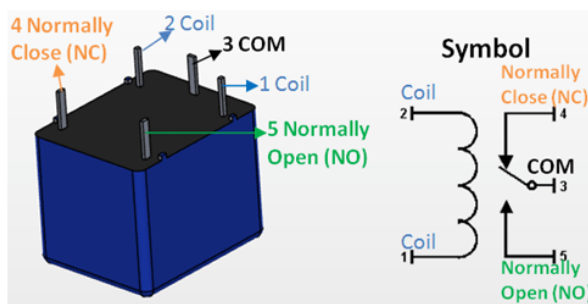- ◆ Logic switching element (i.e. control relay)
- ◆ Current/Voltage amplifier (i.e. power relay)



Electro-Mechanical Relay -2

□ Advantages

- ◆ Electric isolation between the control signal (coil) and the outputs (contacts)
- ◆ Using a small voltage/current to control large voltages/currents
- ◆ Simultaneously control of many different loads (independent circuits possible)


□ Major failure & solutions

- ◆ Failure: Arc generated when the contact is established/broken
- ◆ Solutions: Quick contact/release or arc-suppression circuit

Electro-Mechanical Relay -3




Specifications

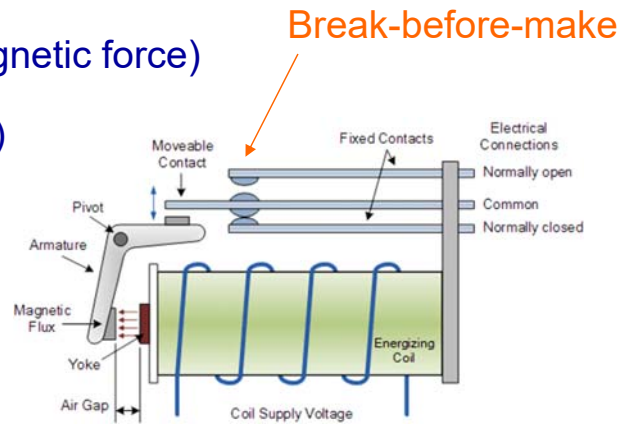- ◆ Coil voltage: DC 5V, 12V, 24V,...; AC 120V, 240V,...
- ◆ Coil current: 10-200 mA (usually)
- ◆ Contact current rating: ??A
- ◆ Contact arrangement: SPDT, DPDT,...
- ◆ Operating time (i.e. electromagnetic force)
- ◆ Release time (i.e. spring force)
- ◆ Lifetime: ??? cycles





Electro-Mechanical Relay -4

Ex: Driving a relay using a NPN BJT

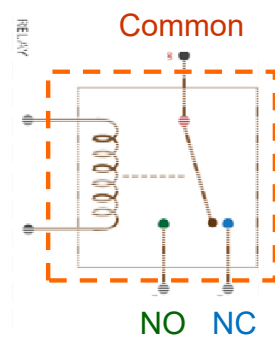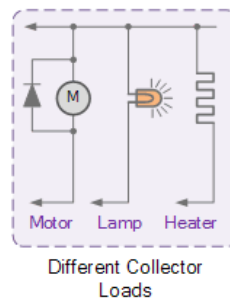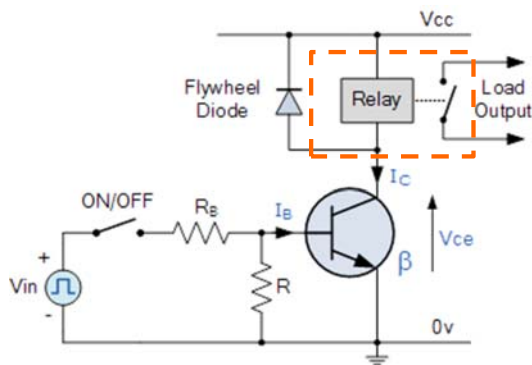


Electro-Mechanical Relay -5


Ex: A RS Flip-flop circuit

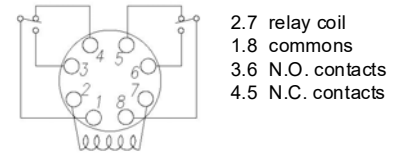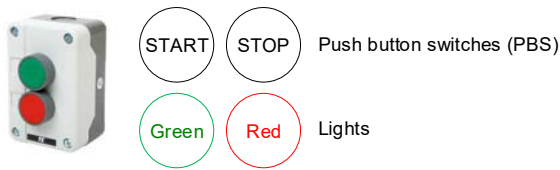


Ladder diagram

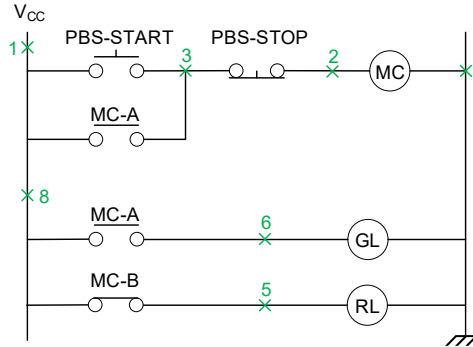

Wiring diagram

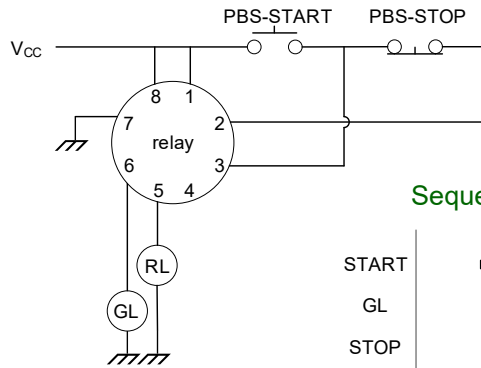





Sequence chart

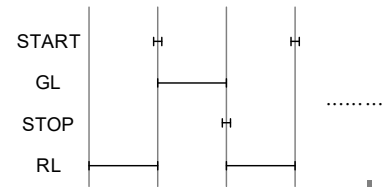

Solid-State Relay -1

Features

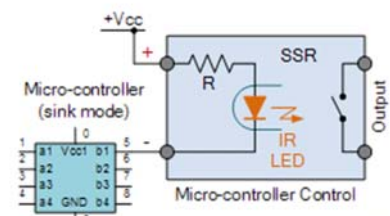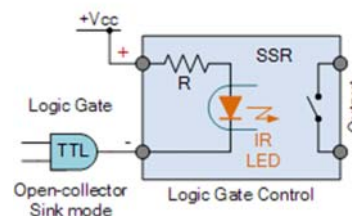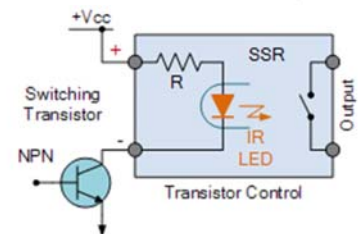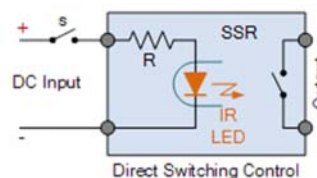- Using the electrical and optical properties of solid state semiconductors to perform its input to output isolation and switching functions
- Unlike EMR, SSR doesn't have moving parts
- Can switch both AC or DC currents





Solid-State Relay -2

- Solid-state relay vs. mechanical relay

- ◆ Pros

- Faster response
- Higher cycle of operation
- Smaller package
- Can be powered by low-power electronic circuits (Ex: TTL)
- Resistant to shock and vibration



Solid-State Relay -3

- Solid-state relay vs. mechanical relay


- ◆ Cons

- Less tolerance to noise, temperature variation, overload
- Requiring stable power supply
- One control switches only one circuit
- Current leakage in OFF state (several mA)
- Usually fails in ON state

Solid-State Switches - 1

□ Devices

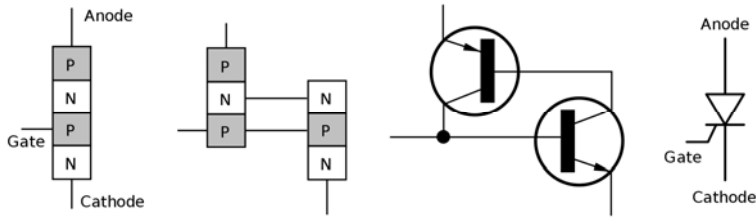- ◆ Diodes
- ◆ Solid-state relay
- ◆ Thyristors (閘流體) or silicon-controlled rectifier (SCR)
 - A device with four layers of P- and N-type materials




- ◆ Triac or bidirectional triode thyristor




Solid-State Switches - 2


◆ BJT

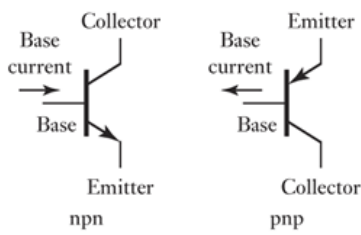


(a)

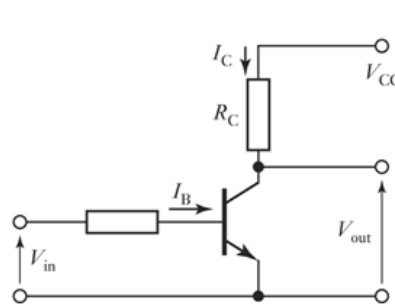

(b)

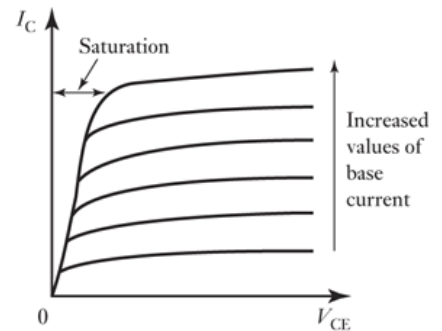


(c)

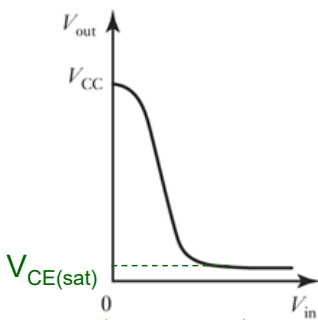


“OFF”

“ON”

(d)

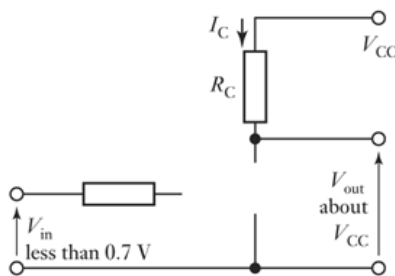

“OFF”

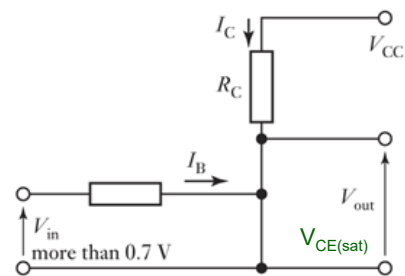


“ON”

(e)


Solid-State Switches -3

◆ BJT

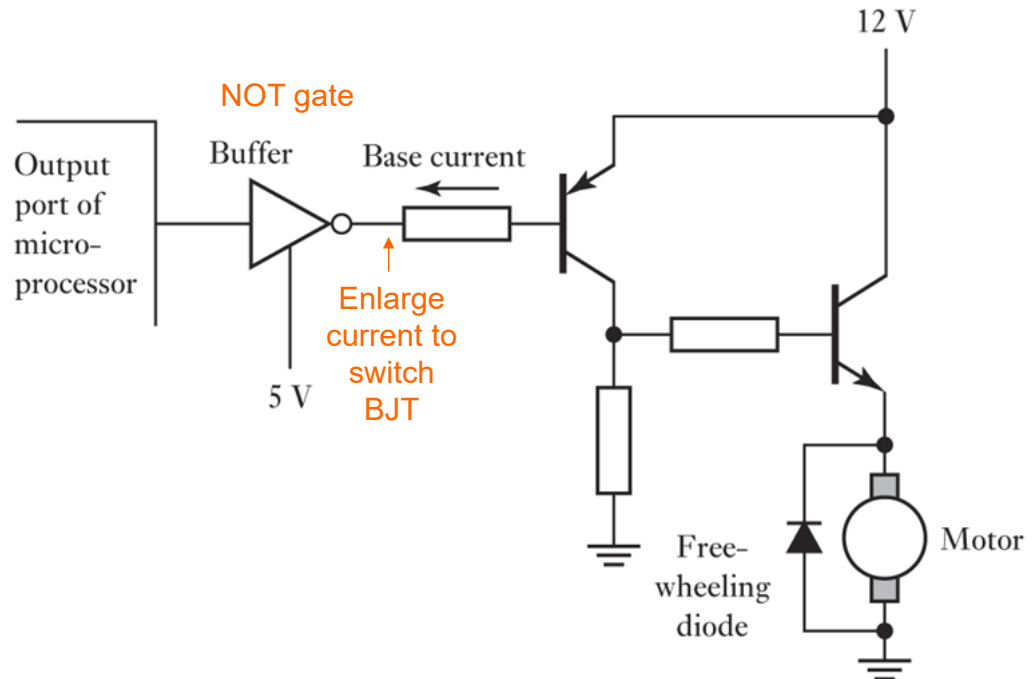

Solid-State Switches -4

◆ MOSFET

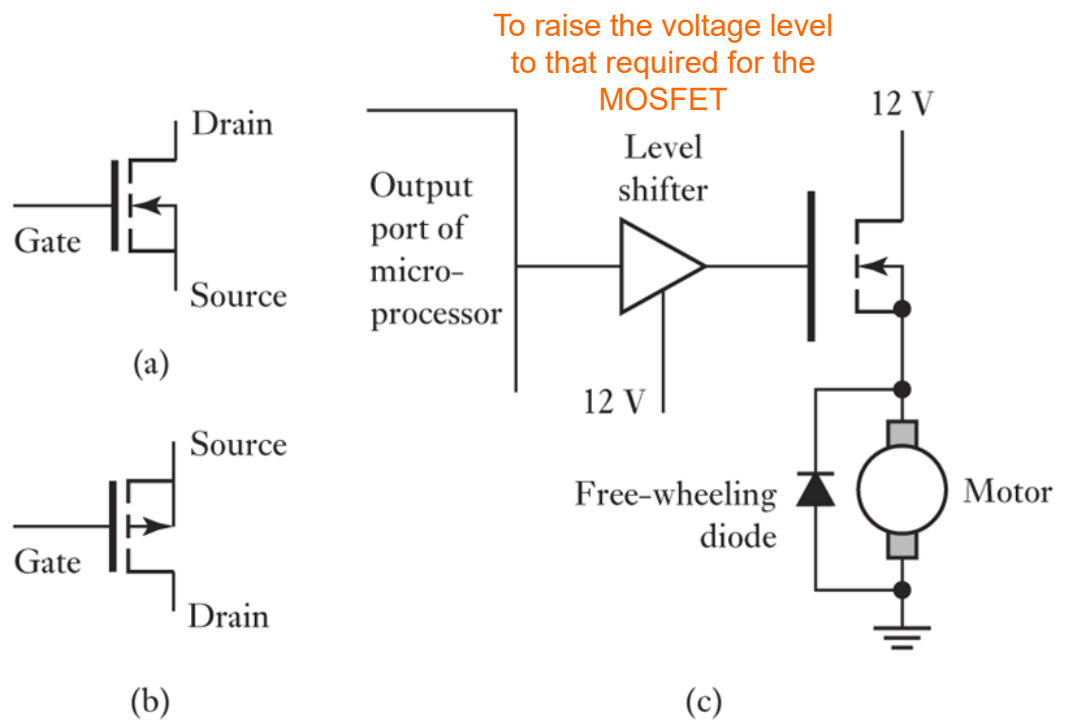

- Questions?

